

Exercise 10


1. (Enhanced Slew Propagation)

Consider following modified slew propagation rules:

$$\begin{aligned}\underline{\text{shape}}(q, \sigma) &:= \min \left\{ \underline{\text{shape}}(e, \sigma) + \nu \cdot (\underline{\text{at}}(e, \sigma) - \underline{\text{at}}(q, \sigma)) \mid e \in \delta^-(q), \sigma \in S(e) \right\}, \\ \overline{\text{shape}}(q, \sigma) &:= \max \left\{ \overline{\text{shape}}(e, \sigma) + \nu \cdot (\overline{\text{at}}(e, \sigma) - \overline{\text{at}}(q, \sigma)) \mid e \in \delta^-(q), \sigma \in S(e) \right\}\end{aligned}$$

with the notation of the standard slew propagation (pages 75–76 in the script) and a constant $\nu \geq 0$. Let $\hat{\lambda}$ and $\hat{\vartheta}$ be global Lipschitz constants of λ_e and ϑ_e over all $e \in E(G)$ and over the whole range Λ of feasible input slews, i.e. $|\lambda_e(s_1) - \lambda_e(s_2)| \leq \hat{\lambda}|s_1 - s_2|$ and $|\vartheta_e(s_1) - \vartheta_e(s_2)| \leq \hat{\vartheta}|s_1 - s_2|$ for all propagation edges $e \in E(G)$ and all $s_1, s_2 \in \Lambda$. Suppose that $\hat{\lambda} < 1$. Show that using $\nu = \frac{1-\hat{\lambda}}{\hat{\vartheta}}$ leads to arrival time values $\overline{\text{at}}(p, \sigma)$ ($\underline{\text{at}}(p, \sigma)$) for each timing node p and each $\sigma \in S(p)$ that are at least (at most) those of any signal σ propagated to p in full path propagation. Full path propagation is defined as the propagation mode where signals with equal origin and transition are **not** merged, i.e. each path is analyzed independently from others. (6 points)

 2. Consider a chain of $n \in \mathbb{N}$ continuously sizable inverters with sizes $x_i \geq L > 0$ ($1 \leq i \leq n$). The $(i+1)$ -th inverter is successor of i -th inverter for $1 \leq i < n$.



Ignore wire delays and assume the RC-delay model from the lecture, i.e. slews and transitions are ignored, and the delay θ_i from the output of inverter $i-1$ to the output of inverter i ($1 \leq i \leq n$) is given by a posynomial

$$\theta_i(x) = \alpha + \frac{\beta}{x_i} C_i$$

where $x = (x_1, \dots, x_n)$, $\alpha \geq 0$, $\beta > 0$, and $C_i = x_{i+1}$ for $i = 1, \dots, n-1$. Furthermore, assume that the start time $\text{at}(0, x)$ of the signal entering the first

inverter (inverter 1) depends linearly on the inverter size ($\text{at}(0, x) = \beta x_1$) and that the last inverter drives a fixed capacitance of $C_n = L$.

Derive a closed formula for the size x_i of the i -th inverter in a solution x of the total delay minimization problem:

$$\min \left\{ \text{at}(0, x) + \sum_{i=1}^n \theta_i(x) \mid x_i \geq L \text{ for all } 1 \leq i \leq n \right\}.$$

(6 points)

The deadline for this exercise is **Tuesday July 1 at 12:15**, before the lecture.