

Exercise Set 2

Exercise 2.1. For $f \in B_n$ let $S_{\text{DNF}}(f)$ be the minimum number of literals needed in any DNF representation of f . Show that $\max\{S_{\text{DNF}}(f) \mid f \in B_n\} \in \Omega(2^n)$.

(5 points)

Exercise 2.2. A Boolean function $f \in B_n$ *depends essentially* on all its variables if for every $1 \leq i \leq n$ the subfunctions $f|_{x_i=0}$ and $f|_{x_i=1}$ are different.

Let $f \in B_n$ be a function that essentially depends on all its variables. Show:

(a) $S_{B_2}(f) \geq n - 1$,

(b) $D_{B_2}(f) \geq \lceil \log_2 n \rceil$.

(5 points)

Exercise 2.3. Let $f \in B_n$ be a Boolean function given as an oracle (i.e. for each $x \in \{0, 1\}^n$ the value $f(x)$ can be computed in $\mathcal{O}(1)$ time). Show that the set $PI(f)$ of all prime implicants can be computed in $\mathcal{O}(n^2 3^n)$ time.

(5 points)

Exercise 2.4. Assume unit B_2 -circuit-delay and zero wire-delay.

- (a) Show that for n inputs with arrival times $t_i \in \mathbb{N}$ ($i = 1, \dots, n$) there are n -ary AND, OR or XOR circuits over B_2 with delay $d \in \mathbb{N}$ if and only if

$$\sum_{i=1}^n 2^{t_i-d} \leq 1.$$

- (b) Provide an algorithm that finds such a circuit in $\mathcal{O}(n \log n)$ time.

(3 + 3 points)

Deadline: April 23rd, before the lecture. The websites for lecture and exercises can be found at:

http://www.or.uni-bonn.de/lectures/ss24/chipss24_ex.html

In case of any questions feel free to contact me at schlomberg@or.uni-bonn.de.